



# CIRCUIT DESIGN WITH HDL

# Course outline

- Chapter 1: Introduction
- Chapter 2: Verilog Language Concepts
- Chapter 3: Structural modeling
- Chapter 4: Behavioral modeling
- **Chapter 5: Finite State machines**
- Chapter 6: Tasks and Functions
- Chapter 7: Functional Simulation/Verification (Testbench)
- Chapter 8: Synthesis of Combinational and Sequential Logic
- Chapter 9: Post-synthesis design tasks
- Chapter 10: VHDL introduction


# Introduction

- Finite State Machines (FSMs):
  - A useful abstraction for digital logic circuits with centralized “states” of operation
  - A main control block of any digital logic circuit
- Three basic components:
  - Combinational logic – next states
  - Sequential logic – store states (current states)
  - Output logic

# FSM types


- There are two types of designing FSM

## Moore type

 

Next state =  $F(\text{current state, inputs})$   
Outputs =  $G(\text{current state})$

## Mealy type

 


Next state =  $F(\text{current state, inputs})$   
Outputs =  $G(\text{current state, inputs})$

# FSM types (con't)


- implement at circuit level

**Moore type**

 

Next state =  $F(\text{current state, inputs})$   
Outputs =  $G(\text{current state})$


**Mealy type**

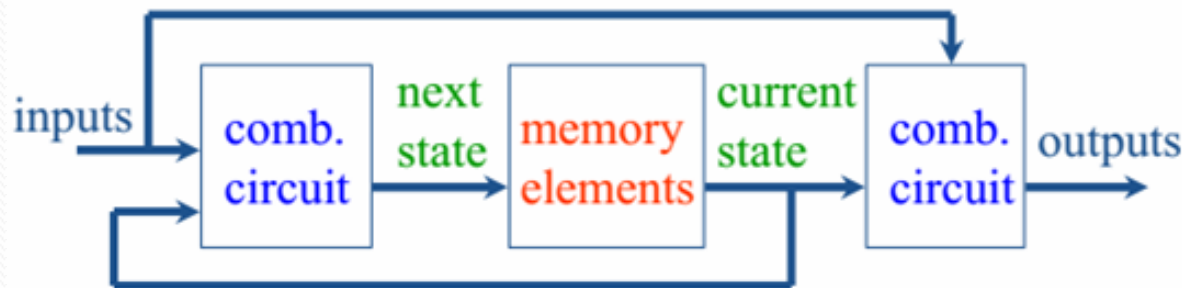

Next state =  $F(\text{current state, inputs})$   
Outputs =  $G(\text{current state, inputs})$


# FSM types (con't)

## Moore type example

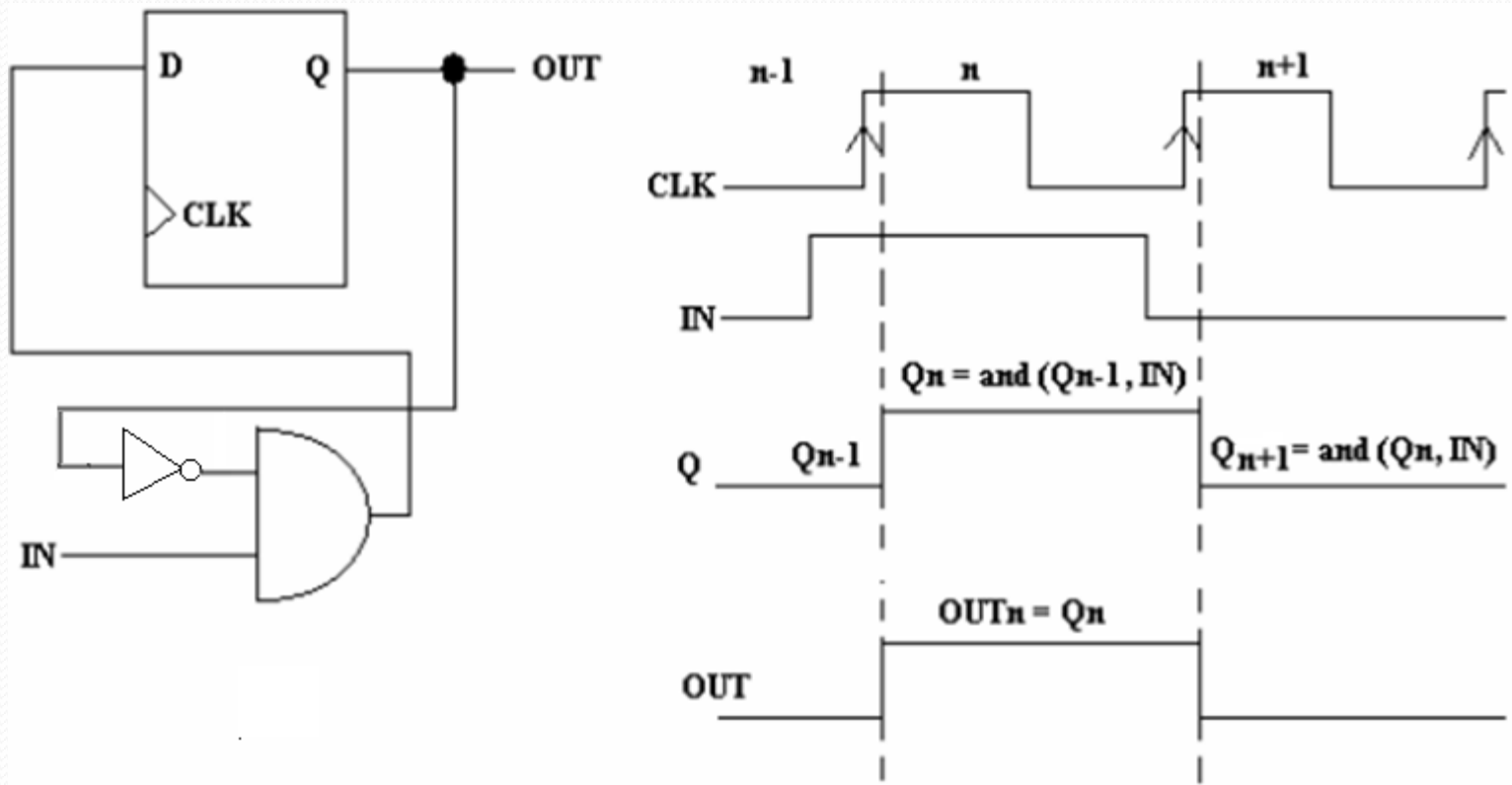

# FSM types (con't)

## Mealy type example

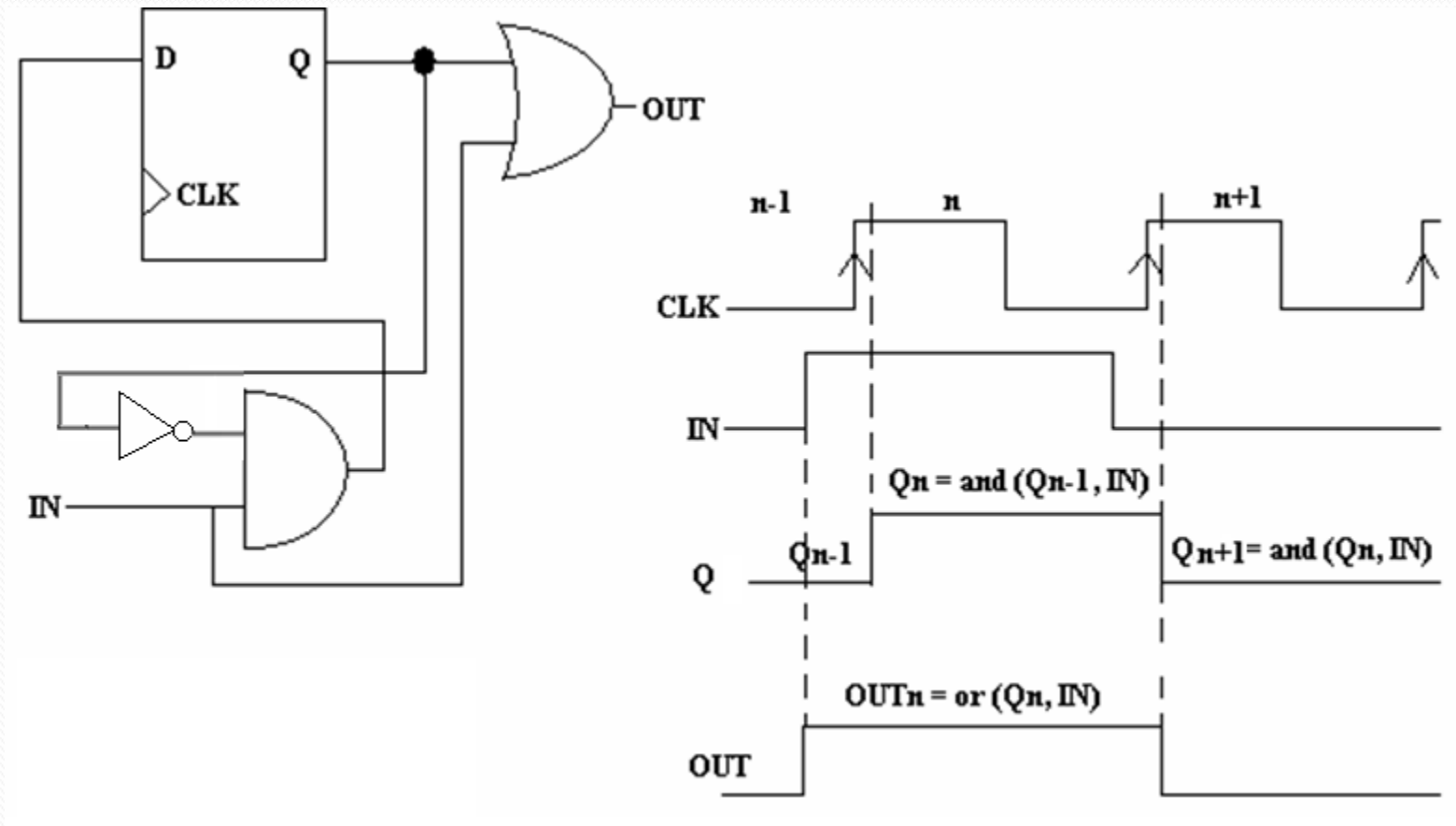

# Constructing State Machines

- **Current state logic**

- Register to hold: *always @(posedge/negedge clock)* block

- **Next state logic**

- State by state case analysis: next state determined by *current state* and given *inputs*

- **Output logic**

- State by state analysis:

- Moore: output determined by current state only

- Mealy: output determined by current state and inputs



# Constructing State Machines (con't)

- Model **FSM**:

- Decide how many states are needed, which transitions are possible from one state to another

*Using constants declaration like **parameter** or **`define** to define name of states in FSM makes code more readable and easy to manage.*

- Reset state
- “always @ (pos/negedge clock)” defines the **current state**
- *Combinational logic* defines the **next state** and **output logic**

# Constructing State Machines (con't)

- **Encoding state style:**
  - **Binary** (usually used)
  - **One hot** (usually used)
  - One cold
  - Almost one hot
  - Almost one cold
  - Gray

# Constructing State Machines (con't)

- **Encoding state style:**

- ❖ **Binary encoding**



- For  $N$  states, use  $\text{ceil}(\log_2 N)$  bits to encode the state with each state represented by unique combination of the bits.
    - Tradeoffs: most efficient use of state registers, but requires more complicated combinational logic to detect when in a particular state.

- ❖ **One-hot encoding**

- For  $N$  states, use  $N$  bits to encode the state where the bit corresponding to the current state is 1, all the others 0.
    - Tradeoffs: more state registers, but after much less combinational logic since state decoding is trivial.

# FSM Coding Style – Simple model

  - Example: 101 detector (**Moore** style)



# FSM Coding Style – Simple model



Example: 101 detector (**Moore** style)

```
module moore_detector (input x, rst, clk, output z);
  `define reset    2'b00
  `define got1     2'b01
  `define got10    2'b10
  `define got101   2'b11
  reg [1:0] current;
  //---Current state and Next state together
  always @ (posedge clk )
    if ( rst ) current <= `reset;
    else
      case ( current )
        reset: begin
          if( x==1'b1 ) current <= `got1;
          else current <= `reset;
        end
```

```
        got1: begin
          if( x==1'b0 ) current <= `got10;
          else current <= `got1;
        end
        got10: begin
          if ( x==1'b1 ) current <= `got101;
          else current <= `reset;
        end
        got101: begin
          if (x==1'b1 ) current <= `got1;
          else current <= `got10;
        end
        default: current <= `reset;
      endcase
  //----- output -----
  assign z = (current==`got101) ? 1 : 0;
endmodule
```

# FSM Coding Style – Simple model

  - Example: **101** detector (**Mealy** style)



# FSM Coding Style – Simple model



- **Example: 101 detector (Mealy style)**

```
module mealy_detector (input x, rst, clk, output z);  
localparam [1:0] reset = 0, got1 = 1, got10 = 2;  
reg [1:0] current;  
  
always @ (posedge clk ) begin  
    if (rst) current <= reset;  
    else  
        case ( current )  
            reset:  
                if( x==1'b1 ) current <= got1;  
                else current <= reset;  
            got1:  
                if( x==1'b0 ) current <= got10;  
                else current <= got1;
```

```
            got10:  
                if( x==1'b1 ) current <= got1;  
                else current <= reset;  
            default:  
                current <= reset;  
        endcase  
    end  
  
    //----- output -----  
    assign z =  
        (current==got10 && x==1'b1) ?1'b1 : 1'b0;  
  
endmodule
```

# FSM Coding Style – Huffman model

  - Example: 101 detector (**Moore** style)





# FSM Coding Style – Huffman model

- **Example: 101 detector (Moore style)**

```
module moore_detector (input x, rst, clk, output reg z);  
  parameter [1:0] reset=0, got1=1, got10=2, got101=3;  
  reg [1:0] p_state, n_state;
```

//---Next state and Output circuit together -----

```
always @ (*) begin  
  case ( p_state )  
    reset: begin  
      if( x==1'b1 ) n_state = got1;  
      else n_state = reset;  
      z = 1'b0;  
    end  
    got1: begin  
      if( x==1'b0 ) n_state = got10;  
      else n_state = got1;  
      z = 1'b0;  
    end  
  end
```

```
    got10: begin  
      if( x==1'b1 ) n_state = got101;  
      else n_state = reset;  
      z = 1'b0;
```

```
    end
```

```
    got101: begin  
      if( x==1'b1 ) n_state = got1;  
      else n_state = got10;  
      z = 1'b1;
```

```
    end
```

```
    default: begin  
      n_state = reset;  
      z = 1'b0;
```

```
    end
```

```
  endcase
```

```
end
```



//----- current state logic-----

```
always@(posedge clk )  
  if ( rst )   p_state <= reset;  
  else        p_state <= n_state;
```

```
endmodule
```

# FSM Coding Style – more modular model

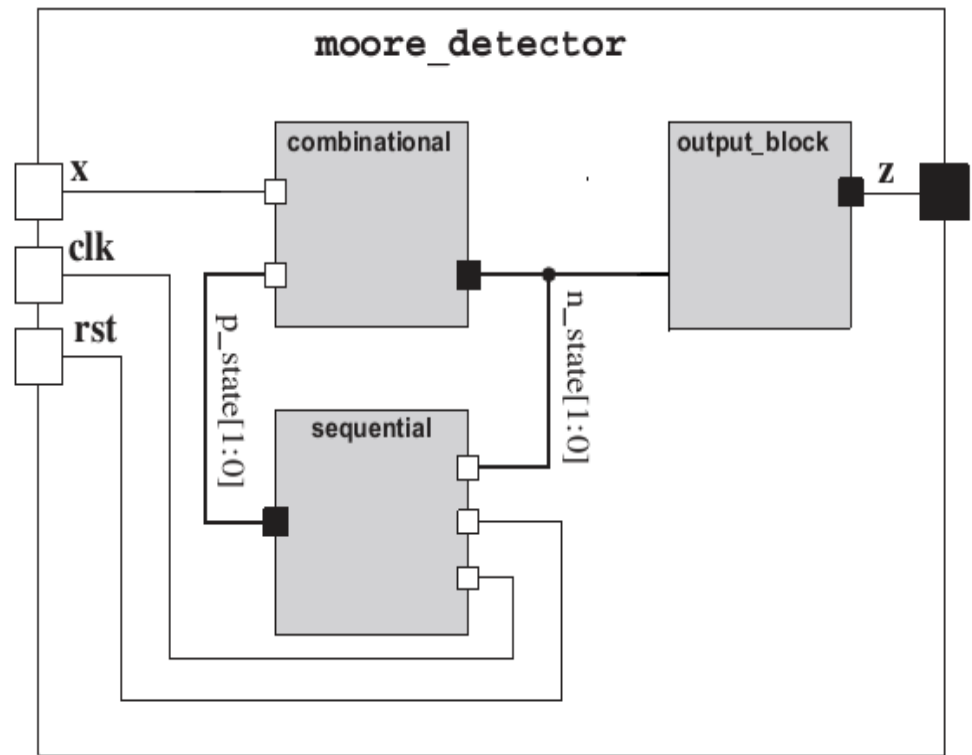 - Example: 101 detector (**Moore** style)



# FSM Coding Style – more modular model

- **Example: 101 detector (Moore style)**

```
module moore_detector( input x, rst, clk, output z);

localparam [1:0] reset=0, got1=1, got10=2, got101=3;
reg [1:0] state, next_state;

//-- Combinational Next State Logic ----
always @(*)
case (state)
reset:
    if (x == 1'b1) next_state = got1;
    else    next_state = reset;
got1:
    if (x == 1'b1) next_state = got1;
    else    next_state = got10;
got10:
    if (x == 1'b1) next_state = got101;
    else next_state = reset;
```

```
got101:
    if (x == 1'b1) next_state = got1;
    else next_state = got10;
default:
    next_state = reset;
endcase // case(state)



//--- State FF Transition (current state)-----
always @(posedge clock)
    if (reset == 1'b0)
        state <= reset;
    else
        state <= next_state;

//---- Combinational Output Logic ---
assign z = (state == got101) ? 1: 0;

endmodule
```

# FSM Coding Style – more modular model

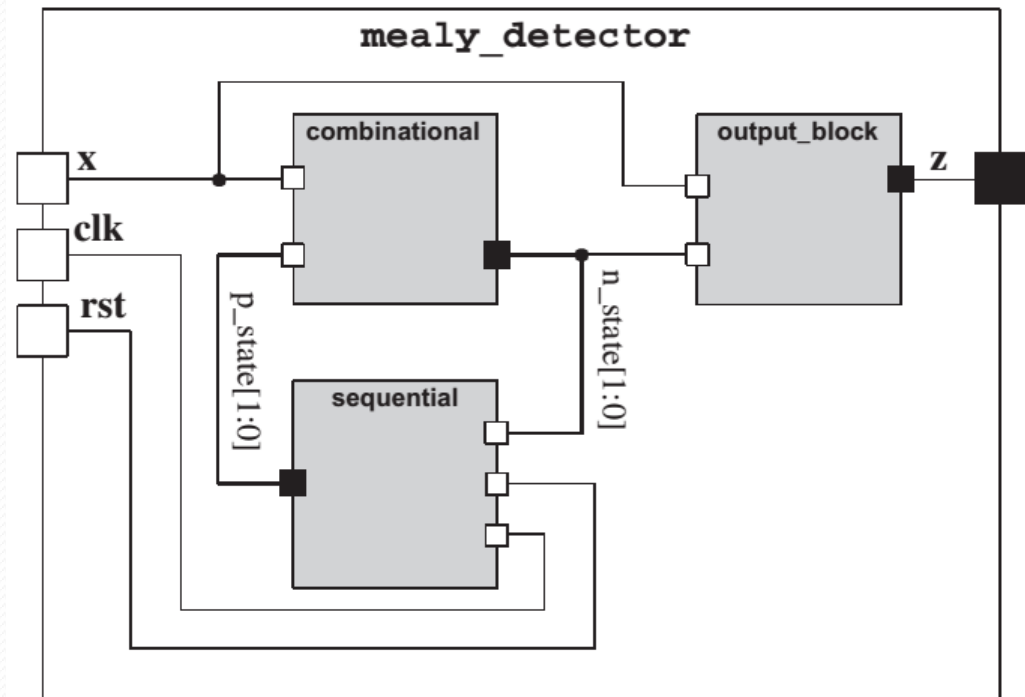 - Example: 101 detector (**Mealy** style)



# FSM Coding Style – more modular model

- **Example: 101 detector (Mealy style)**

```
module moore_detector (input x, rst, clk,  
                      output z);  
parameter [1:0] reset=0, got1=1, got10=2;  
reg [1:0] state, next_state;
```

```
//---Combinational Next State Logic---
```

```
always @(*)
```

```
  case (state)
```

```
    reset:
```

```
      if (x) next_state = got1;  
      else next_state = reset;
```

```
    got1:
```

```
      if (x) next_state = got1;  
      else next_state = got10;
```

```
    got10:
```

```
      if (x) next_state = got1;  
      else next_state = reset;
```

```
default:
```

```
  next_state = reset;
```

```
endcase // case(state)
```

```
//---State FF Transition----
```

```
always @(posedge clock)
```

```
  if (reset == 1'b0)
```

```
    state <= reset;
```

```
  else
```

```
    state <= next_state;
```

```
//---Combinational Output Logic---
```


```
assign z =
```

```
  (state == got10) && (x == 1);
```

```
endmodule
```
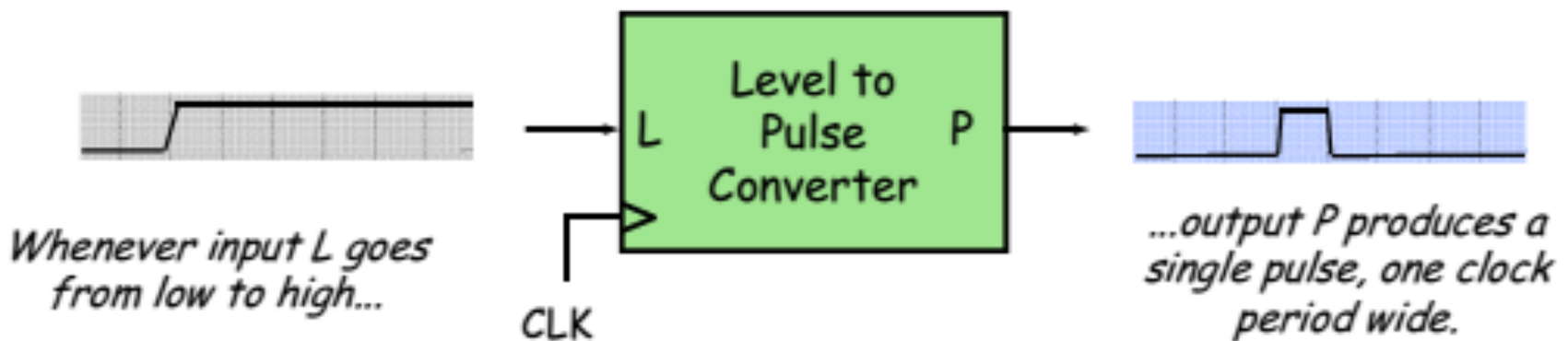
# Design Example – Level-to-Pulse

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
  - Buttons and switches pressed by humans for arbitrary periods of time
  - Single-cycle enable signals for counters




Source: MIT




# Asynchronous Inputs in Sequential System

What about external signals?

 

*Can't guarantee setup and hold times will be met!*

 When an asynchronous signal causes a setup/hold violation...





**Q: Which cases are problematic?**
  
# Asynchronous Inputs in Sequential System

**All of them can be,** if more than one happens simultaneously within the same circuit.

*Idea: ensure that external signals directly feed **exactly one** flip-flop*




This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?


 
# Asynchronous Inputs in Sequential System

- Preventing metastability turns out to be an impossible problem
- Solution to metastability: allow time for signal to stabilize




How many registers are necessary?

- Depend on many design parameters (clock speed, design speed,...)
- *A pair of synchronization registers is sufficient*

Source: MIT

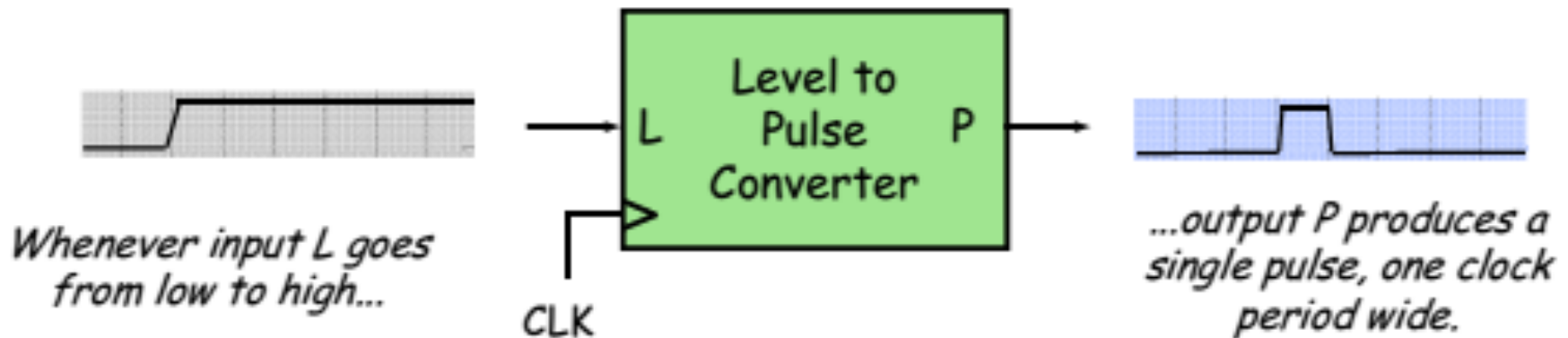
# Design Example – Level-to-Pulse

- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
  - Buttons and switches pressed by humans for arbitrary periods of time
  - Single-cycle enable signals for counters




# Design Example (cont.)

- Block diagram of desired system:

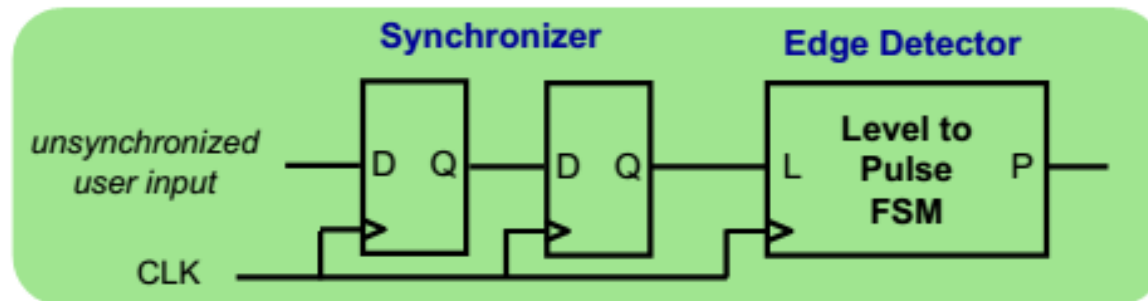


 - State transition diagram** is a useful FSM representation and design aid



 
# Design Example (cont.) – Moore FSM

Transition diagram is readily converted to a state transition table (just a truth table)




Current t State		In	Next State		Out
$S_1$	$S_0$	$L$	$S_1^+$	$S_0^+$	$P$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

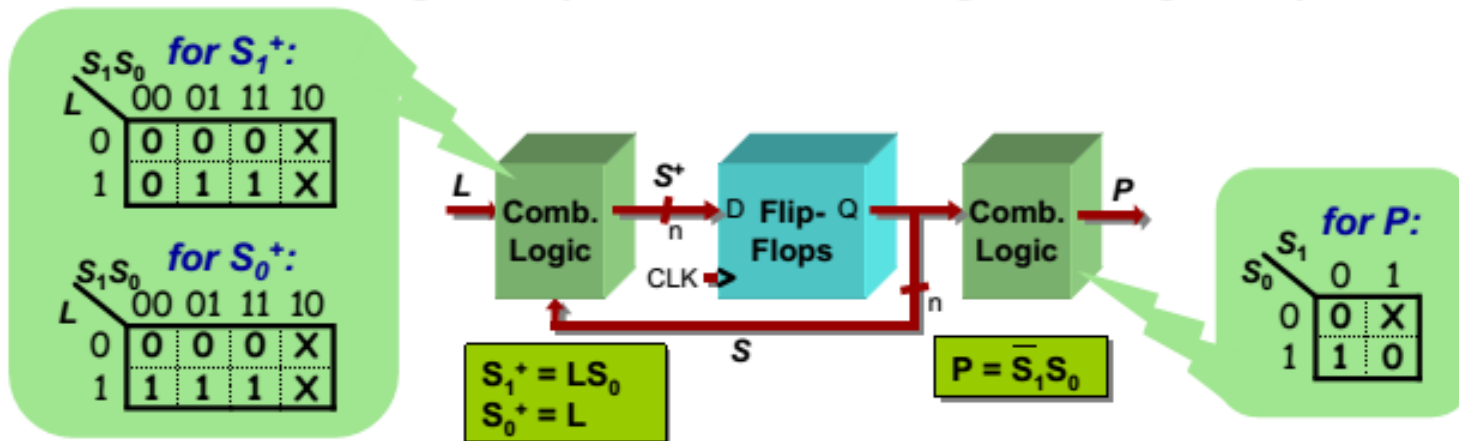- Combinational logic may be derived using Karnaugh maps




Source: MIT

# Design Example (cont.) – Moore FSM

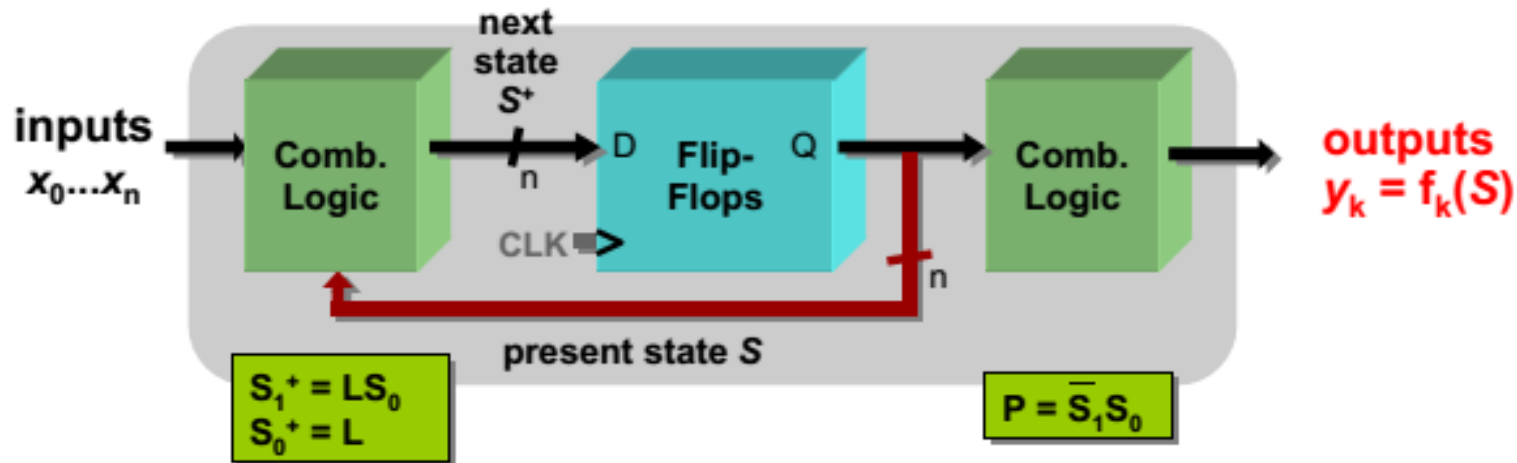

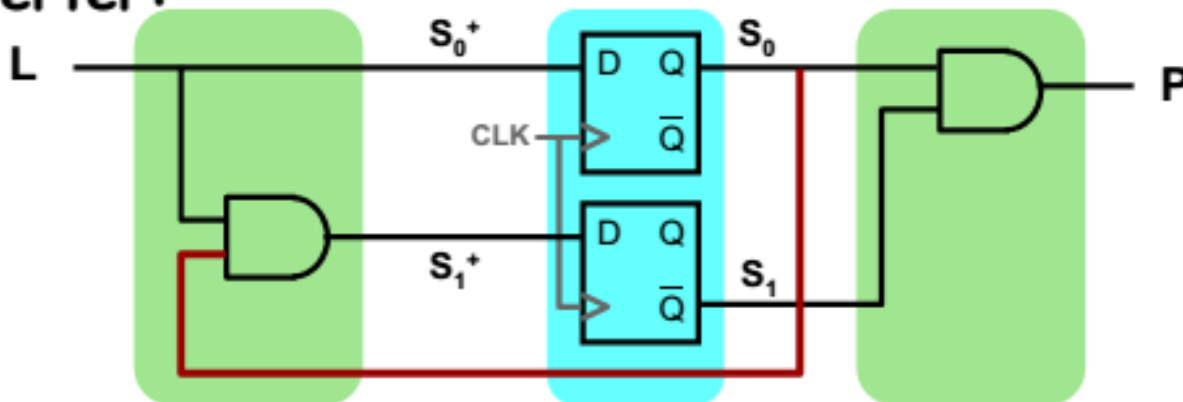
Moore FSM circuit implementation of level-to-pulse converter:




Source: MIT




# Design Example (cont.) – Mealy FSM

 

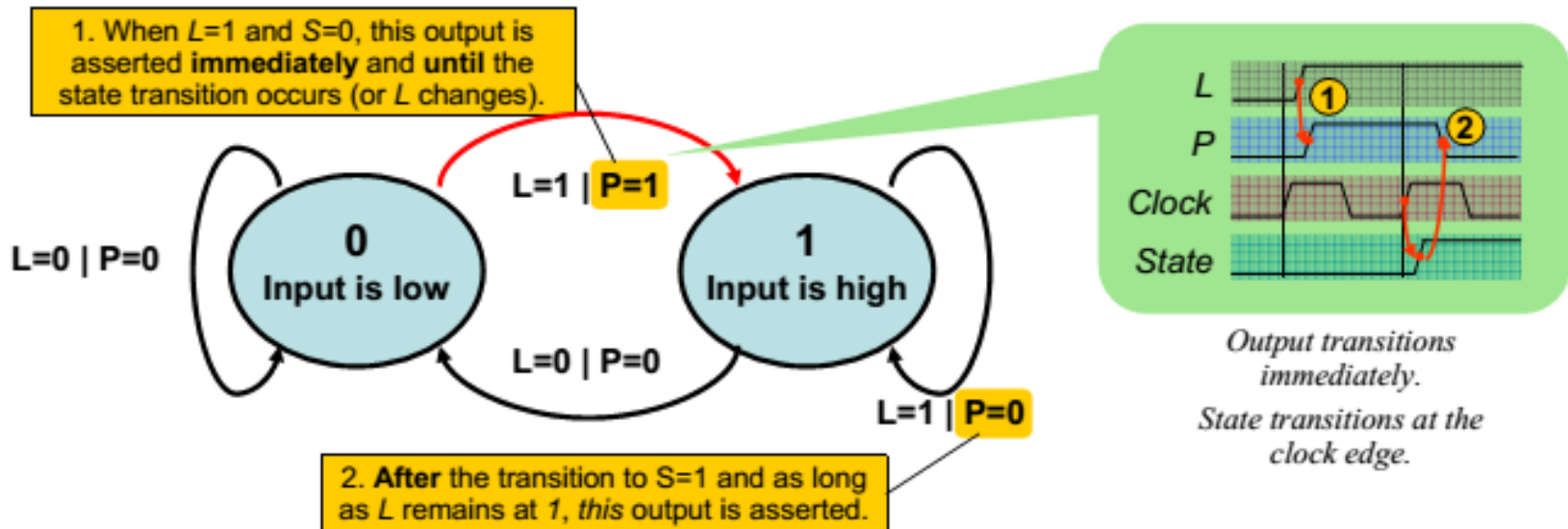- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




# Design Example (cont.) – Mealy FSM

 

Pres. State	In	Next State	Out
<i>S</i>	<i>L</i>	<i>S</i> <sup>+</sup>	<i>P</i>
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

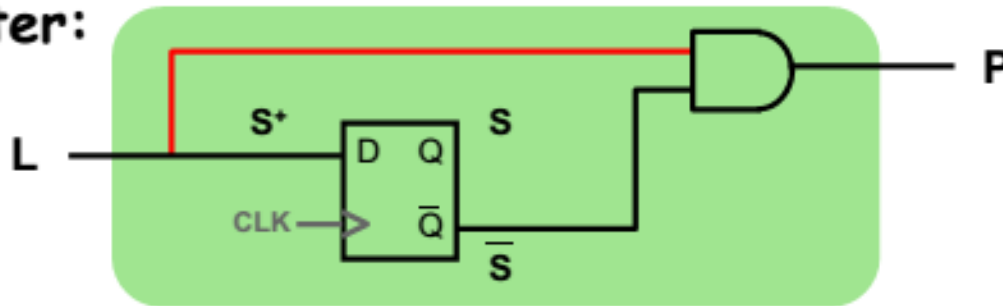Mealy FSM circuit implementation of level-to-pulse converter:



- FSM's state simply remembers the previous value of *L*
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions

Source: MIT

# Typical Example of FSM


- Objectives:
  - Build an electronic combination lock with a reset button, two number buttons – 0 and 1, and an unlock output.
  - The unlock code should be 01011
- Step:
  1. Design lock FSM: block diagram, state transitions
  2. Write verilog module(s) for FSM




Source: MIT



# STEP 1A - Block Diagram

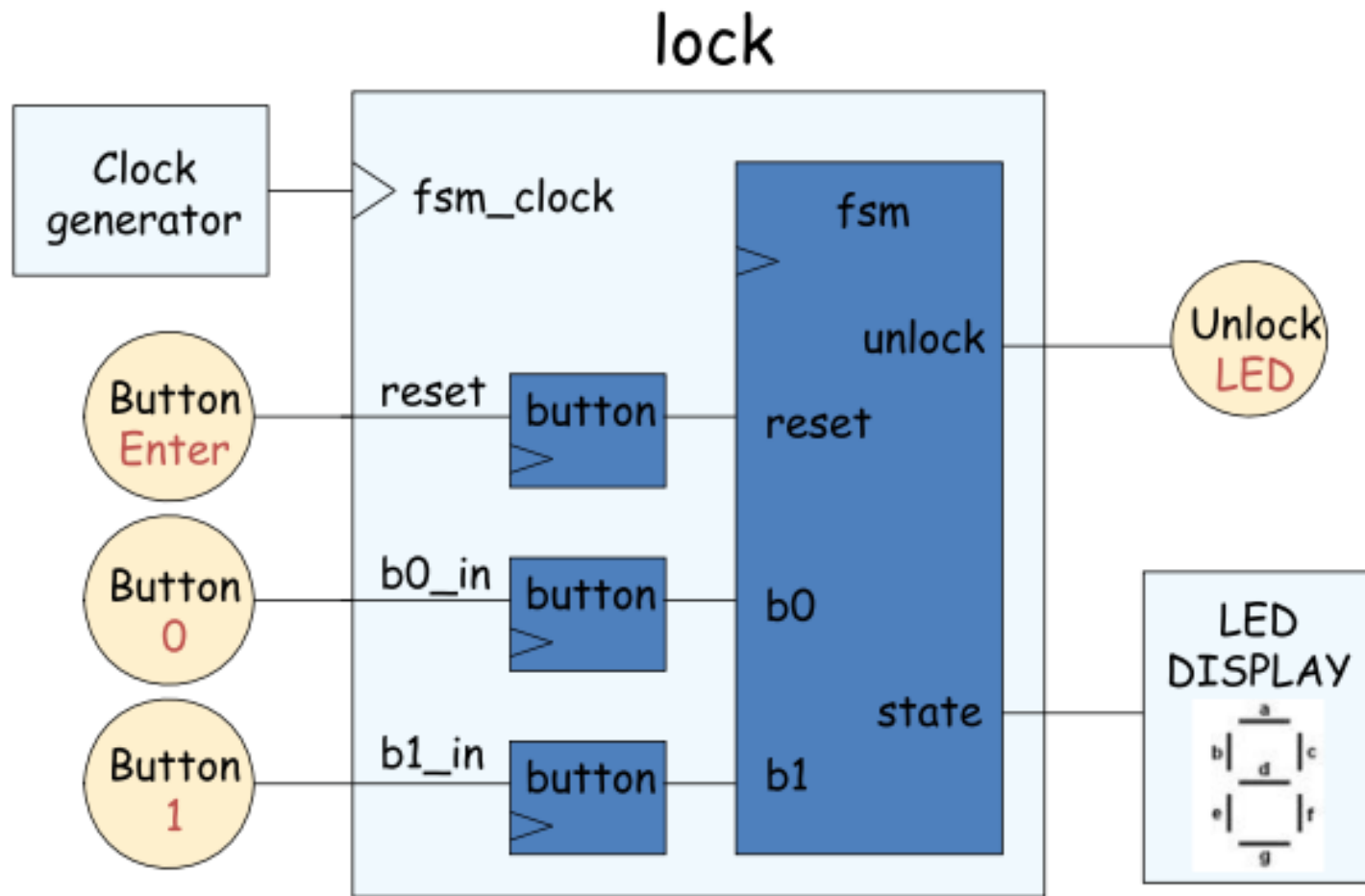

# STEP 1B – State Transition Diagram

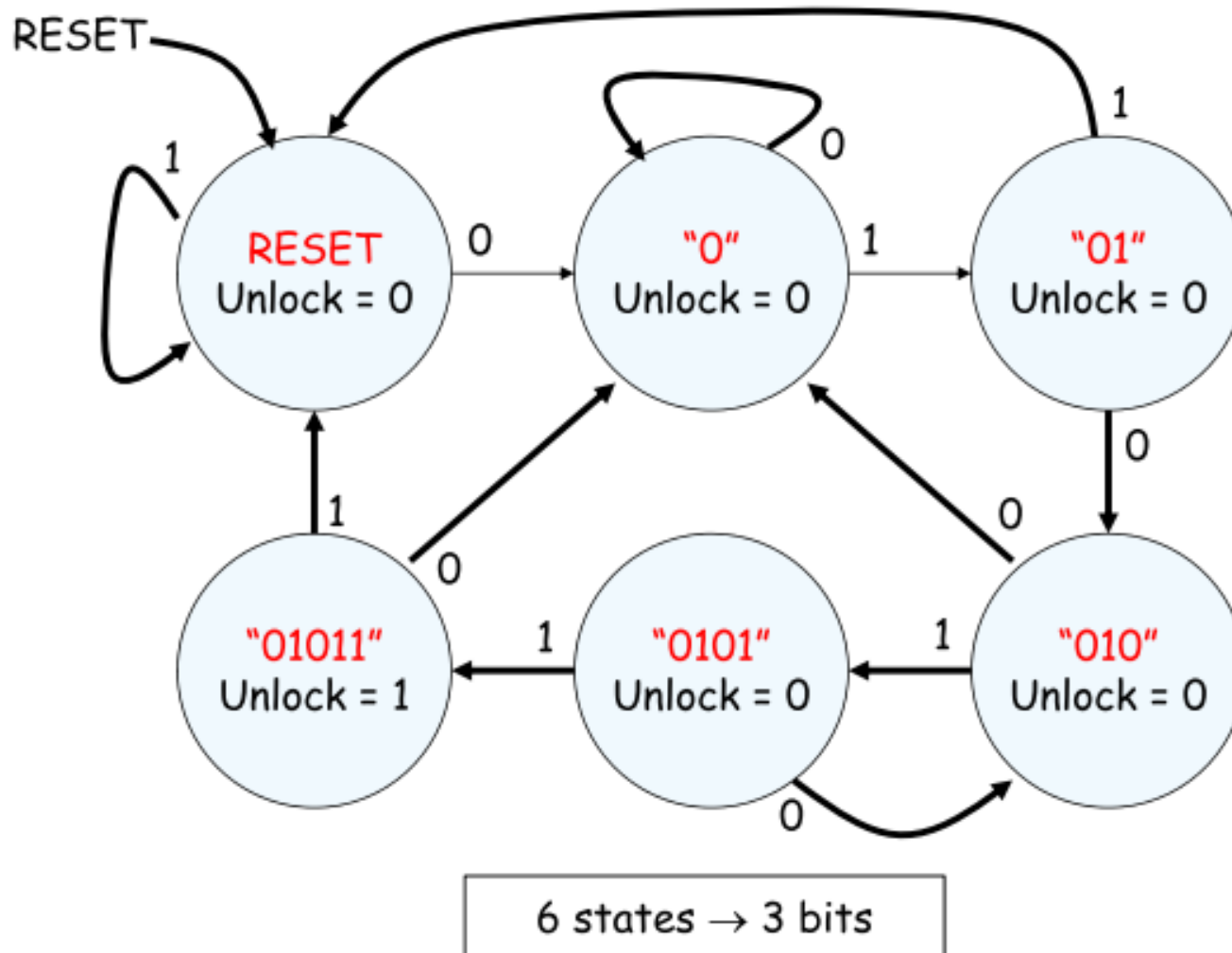

Source: MIT

# STEP 2 – Write Verilog

```
module lock(input clk,reset_in,b0_in,b1_in,  
            output out);
```

```
// synchronize push buttons, convert to pulses
```

```
// implement state transition diagram
```

```
reg [2:0] state,next_state;
```

```
always @(*) begin
```

```
    // combinational logic!
```

```
    next_state = ???;
```

```
end
```

```
// current state
```

```
always @(posedge clk) state <= next_state;
```

```
// generate output
```

```
assign out = ???;
```

```
// debugging?
```

```
endmodule
```

Source: MIT

# STEP 2A – Synchronize Buttons

```
// button
// push button synchronizer and level-to-pulse converter
// OUT goes high for one cycle of CLK whenever IN makes a
// low-to-high transition.
```

```
module button(
  input clk,in,
  output out
);
```

```
  reg r1,r2,r3;
```

```
  always @(posedge clk)
```

```
  begin
```

```
    r1 <= in;    // first reg in synchronizer
```

```
    r2 <= r1;    // second reg in synchronizer, output is in sync!
```


```
    r3 <= r2;    // remembers previous state of button
```

```
  end
```

```
  // rising edge = old value is 0, new value is 1
```

```
  assign out = ~r3 & r2;
```

```
endmodule
```

 


# STEP 2B – State Transition Diagram and Output

```
parameter S_RESET = 0; // state assignments
parameter S_0 = 1;
parameter S_01 = 2;
parameter S_010 = 3;
parameter S_0101 = 4;
parameter S_01011 = 5;
```

```
reg [2:0] state, next_state;
always @(*) begin
    // implement state transition diagram
    if (reset) next_state = S_RESET;
    else case (state)
        S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
        S_0:      next_state = b0 ? S_0 : b1 ? S_01 : state;
        S_01:     next_state = b0 ? S_010 : b1 ? S_RESET : state;
        S_010:    next_state = b0 ? S_0 : b1 ? S_0101 : state;
        S_0101:   next_state = b0 ? S_010 : b1 ? S_01011 : state;
        S_01011: next_state = b0 ? S_0 : b1 ? S_RESET : state;
        default:  next_state = S_RESET; // handle unused states
    endcase
end

 always @(posedge clk) state <= next_state;
```



**// it's a Moore machine!**

```
assign out = (state == S_01011);
```

Source: MIT





# STEP 2 – Final Implementation Verilog

```
module lock(input clk,reset_in,b0_in,b1_in,
            output out );

    wire reset, b0, b1; // synchronize push buttons, convert to pulses
    button b_reset(clk,reset_in,reset);
    button b_0(clk,b0_in,b0);
    button b_1(clk,b1_in,b1);

    parameter S_RESET = 0; parameter S_0 = 1; // state assignments
    parameter S_01 = 2; parameter S_010 = 3;
    parameter S_0101 = 4; parameter S_01011 = 5;

    reg [2:0] state,next_state;
    always @(*) begin // implement state transition diagram
        if (reset) next_state = S_RESET;
        else case (state)
            S_RESET: next_state = b0 ? S_0 : b1 ? S_RESET : state;
            S_0:      next_state = b0 ? S_0 : b1 ? S_01 : state;
            S_01:     next_state = b0 ? S_010 : b1 ? S_RESET : state;
            S_010:    next_state = b0 ? S_0 : b1 ? S_0101 : state;
            S_0101:   next_state = b0 ? S_010 : b1 ? S_01011 : state;
            S_01011:  next_state = b0 ? S_0 : b1 ? S_RESET : state;
            default:  next_state = S_RESET; // handle unused states
        endcase
    end
    always @ (posedge clk) state <= next_state;

    assign out_ = (state == S_01011); // assign output: Moore machine
endmodule
```

Source: MIT



# Real FSM Security System



Source: MIT



# Tips on FSM

- ❖ Don't forget to handle the “**default**” for **case** statement
- ❖ Use *two different **always** blocks* for *next state* and *current state* circuit

Can do it in one big block but not as clear

- ❖ Outputs can be a mix of combin. and seq.

**Moore** machine: Output only depends on current state

**Mealy** machine: Output only depends on current state and inputs