
UNIVERSITY OF INFORMATION TECHNOLOGY

COMPUTER ENGINEERING

REPORT LAB3 VERILOG DESIGN FSM AND SRAM

Student: Trương Thiên Quý

Student code: 23521321

Table of Contents


A. FSM:	2
1. Request:.....	2
2. Diagram:	2
3. Verilog Code:.....	3
4. Simulation:.....	4
B. SRAM:	5
1. Request:.....	5
2. Verilog Code:.....	5
3. <i>Simulation</i>	6

A. FSM:

1. Request:

Sử dụng ngôn ngữ Verilog HDL thiết kế một mạch tuần tự theo mô hình máy trạng thái kiểu Moore. Hệ tuần tự này có chức năng phát hiện 3 bit ngõ vào (X) liên tiếp có giá trị là 010 thì ngõ ra $Z = 1$.

2. Diagram:

 


3. Verilog Code:

```
1 module FSM(Output, Current_State, Input, Reset, CLK);
2 //define_IO
3 input Input, Reset, CLK;
4 output reg Output;
5
6 //define_wire/reg
7 output reg [1:0] Current_State;
8 reg [1:0] Next_State;
9 //body
10 always @(posedge CLK or posedge Reset) begin
11     if(Reset)
12         Current_State <= 2'b00;
13     else
14         Current_State <= Next_State;
15 end
16
17 always @(Input or Current_State) begin
18     case (Current_State)
19     2'd0: begin
20         if (~Input)
21             Next_State <= 2'd1;
22         else
23             Next_State <= 2'd0;
24         Output <= 0;
25     end
26     2'd1: begin
27         if (Input)
28             Next_State <= 2'd2;
29         else
30             Next_State <= 2'd1;
31         Output <= 0;
32     end
33     2'd2: begin
34         if (~Input)
35             Next_State <= 2'd3;
36         else
37             Next_State <= 2'd0;
38         Output <= 0;
39     end
40     2'd3: begin
41         Next_State <= 2'd0;
42         Output <= 1;
43     end
44     default: begin
45         Next_State <= 2'd0;
46         Output <= 0;
47     end
48 endcase
49 end
50 endmodule
```

Explain:

- There are 4 states perform for 4 cases:
 - State 1 (00): the chain we must recognize is 010, when the first input equal 0 the it changes to state 2 (01), now we have had the first bit of chain, else it still State 0 (mean don't have any fit bit). Output is 0.
 - State 2 (01): we already have bit 0 from State 1, we must recognize 010, so if the next input is 1, it changes to State 3(10), else it still in State 0 because the input equal 0 (the first bit of chain). Output is 0.
 - State 3(10): we already have 01 after state 2, and we must recognize 010, so to change to state 4 (11), the next input must be 0. Else it comebacks state 0(01) because if input is 1, the chain now is 011, very different with the chain we must recognize (010). Output is 0.
 - State 4(11): we already have 010 after state 3, if the next input is 0, we will have 0100, easy to see that the last bit is 0 – the first bit in chain 010, so it change to state 2(02). Else if the next input is 1, we will have 0101, similar the previous, we easy to see 2 last bit is 01 – 2 first bit in chain 010, so it change to state 3 (01). We completed recognize 010, so output is 1.
- Begin, the state is 00, depend on input it will change to different state.

4. Simulation:

 

B. SRAM:

1. Request:

Sử dụng ngôn ngữ Verilog HDL, hiện thức thiết kế bộ nhớ dữ liệu (Data Memory) SRAM có các tín hiệu sau: Address[31:0], WriteData[31:0], ReadData[31:0], WriteEn, ReadEn và viết testbench kiểm tra chức năng trên phần mềm mô phỏng ModelSim.

2. Verilog Code:

```
1 module SRAM (Address, WriteData, ReadData, WriteEn, ReadEn);
2 //define_IO
3 input [31:0] Address, WriteData;
4 output reg [31:0] ReadData;
5 input WriteEn, ReadEn;
6
7 //define_wire/reg
8 reg [31:0] memory [4294967295:0]; // Khai báo một mảng 2D 255x32
9
10 //body
11 always begin
12     if (WriteEn) begin
13         memory[Address] <= WriteData; // Ghi dữ liệu vào địa chỉ chỉ định khi WriteEn được kích hoạt
14         ReadData <= 32'dZ;
15     end
16     else if (ReadEn) begin
17         ReadData <= memory[Address]; // Đọc dữ liệu từ địa chỉ chỉ định khi ReadEn được kích hoạt
18     end
19 end
20
21 endmodule
```

Explain:

- First we check WriteEn signal. If it equals 1, SRAM only perform write function, now output = Z.
- After that, if WriteEN signal equal 0, we check ReadEN signal, ef ReadEN signal equal 1, SRAM only perform write function, now output = data in the input address (if in that address don't have data, output equal X). Else do nothing.

3. Simulation

