



DIGITAL CIRCUIT DESIGN WITH HDL

Course outline

- Chapter 1: Introduction
- Chapter 2: Verilog Language Concepts
- Chapter 3: Structural modeling
- Chapter 4: Behavioral modeling
- Chapter 5: Finite State machines
- Chapter 6: Tasks and Functions
- Chapter 7: Functional Simulation/Verification (Testbench)
- **Chapter 8: Synthesis of Combinational and Sequential Logic**
- Chapter 9: Post-synthesis design tasks
- Chapter 10: VHDL introduction

Ref: Michael D. Ciletti_Advanced Digital Design with the Verilog HDL– Chapter 6

Task of the designer

Understand how to synthesize combinational logic

Understand how to synthesize sequential logic

Understand how language constructs synthesize

Anticipate the results of synthesis

Adhere to style conventions


- Understanding how to write synthesis-friendly Verilog model is the key to automated design methods.

Synthesis tool


- Synthesis tools perform many tasks:
 - Detect and eliminate redundant logic
 - Detect combination feedback loops
 - Exploit don't care condition
 - Detect unused states
 - Detect and collapse equivalent states
 - Synthesize optimal, technology mapping
 - ...

Modified Y-chart

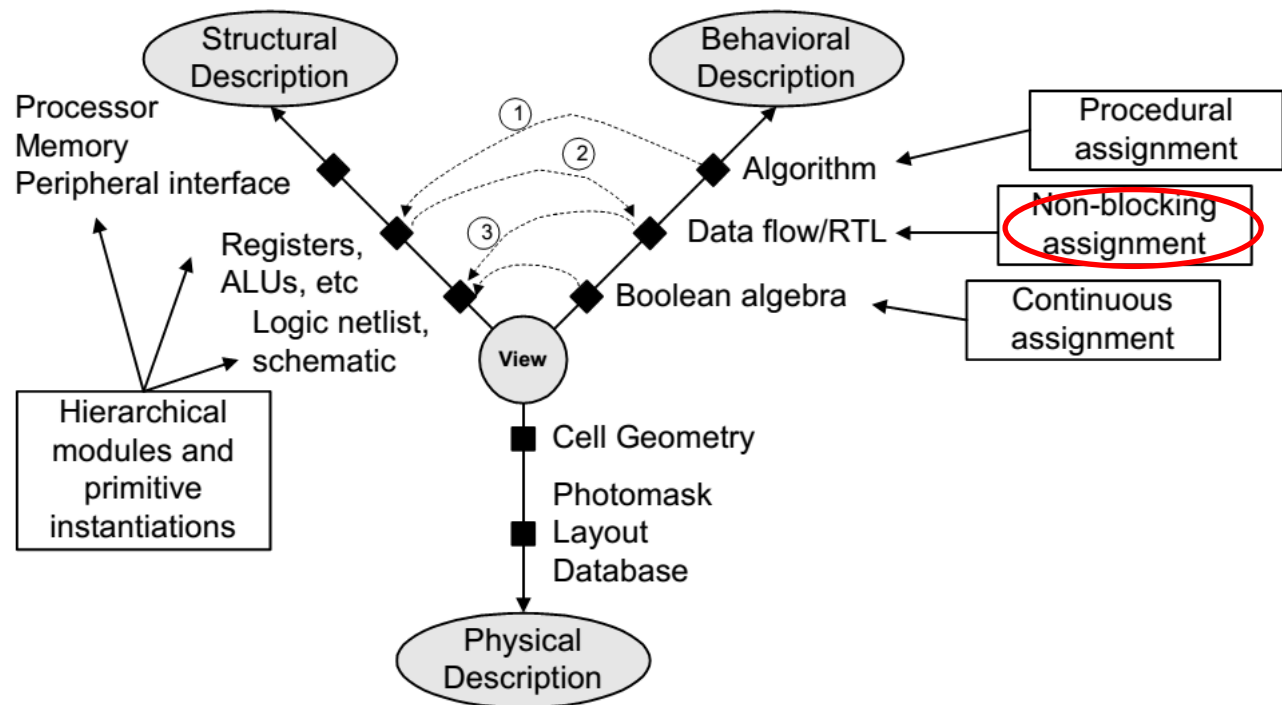Synthesis creates a sequence of transformations between views of a circuit, from a higher level of abstraction to a lower one, with each step leading to a more detailed description of the physical reality.



Synthesis tool organization

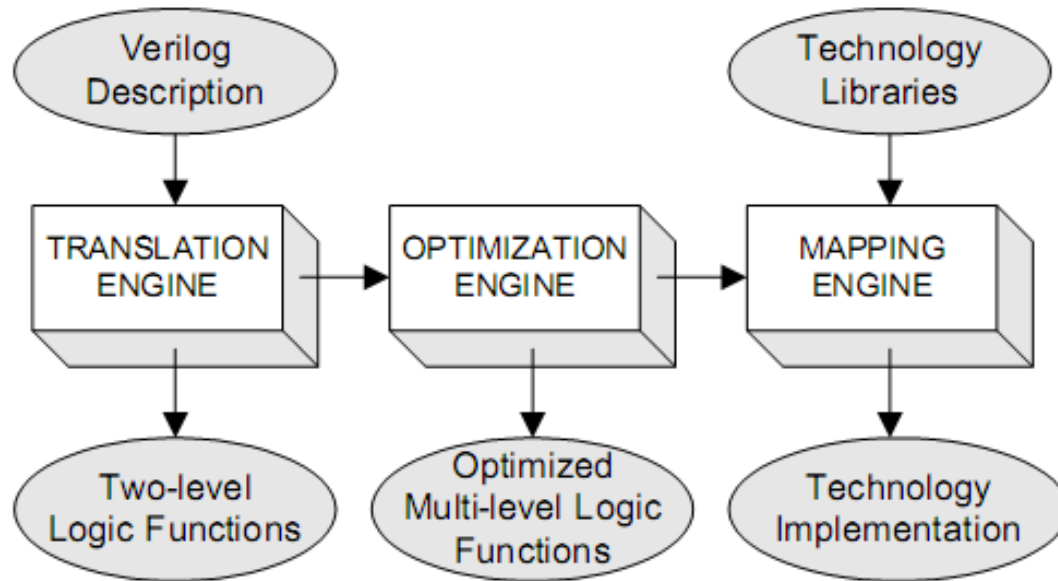

Design Goals: Functionality, area, timing, testability



- Optimization: with logic transformation (ex: Decomposition, Factoring, Extraction, Substitution...)

Decomposition

- Decompose a function into new nodes
- Re-use the new nodes in fanout paths

$$F = abc + abd + a'b'c' + b'c'd'$$

Two-level logic!

  


$$F = XY + X'Y'$$

$$X = ab$$


$$Y = c + d$$

Factoring

$$F = ac + ad + bc + bd + e$$

 

$$F = (a + b)(c + d) + e$$

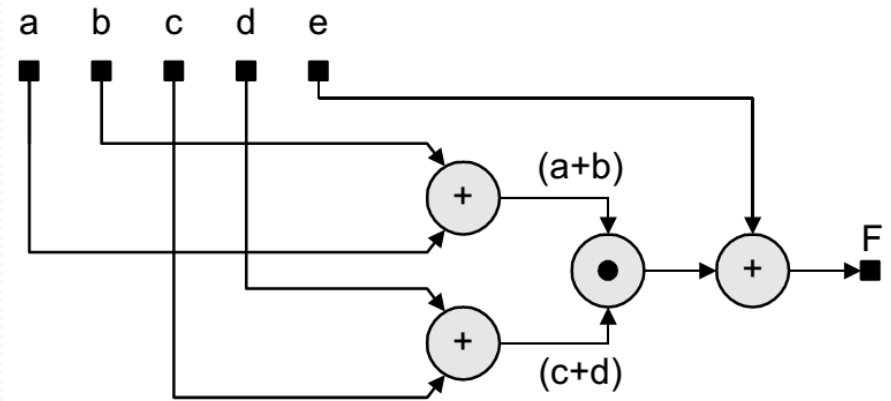

Synthesis of Combinational Logic

Options:

- Netlist of primitives
- User-defined primitive
- Continuous assignments
- Level-sensitive cyclic behavior
- Procedural continuous assignment (***assign ... deassign***)


Some EDA vendors do not support synthesis of UDP and assign...deassign

Synthesis: Netlist of Primitives


Example:

```
module boole_opt (y_out1, y_out2, a, b, c, d, e);  
  output y_out1, y_out2;  
  input a, b, c, d, e;  
  
  and (y1, a, c);  
  and (y2, a, d);  
  and (y3, a, e);  
  or (y4, y1, y2);  
  or (y_out1, y3, y4);  
  and (y5, b, c);  
  and (y6, b, d);  
  and (y7, b, e);  
  or (y8, y5, y6);  
  or (y_out2, y7, y8);  
endmodule
```

Synthesis: Netlist of Primitives

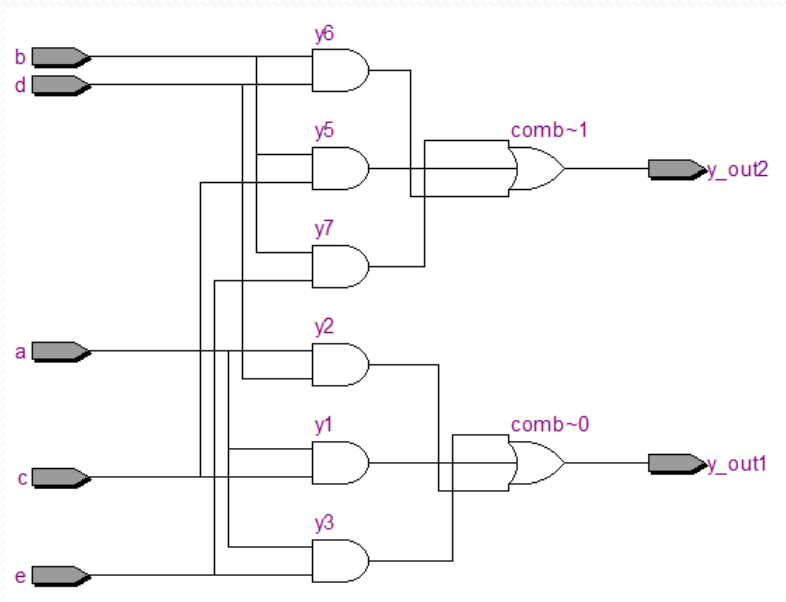

Quartus synthesis result

 


Another synthesis result

- Loại bỏ những dư thừa
- Bảo đảm mạch nhỏ nhất


Synthesis: Continuous Assignment

- Built-in operators have physical counterparts
- Continuous assignment statements are synthesizable
- Will produce (1) combinational logic, (2) latch, (3) three-state output

```
module or_nand (y, enable, x1, x2, x3, x4);  
  output y;  
  input   enable, x1, x2, x3, x4;  
  
  assign y = ~(enable & (x1 | x2) & (x3 | x4));  
endmodule
```

 

Quartus synthesis result

 


Another synthesis result


Synthesis: Continuous Assignment

Synthesis: conditional operator in continuous assignment

```
module udp(y, select, sig_G, sig_max, sig_a, sig_b);  
output y;  
input select, sig_G, sig_max, sig_a, sig_b;  
assign y = (select == 1) || (sig_G == 1) || (sig_max == 0) ? sig_a : sig_b;  
endmodule
```

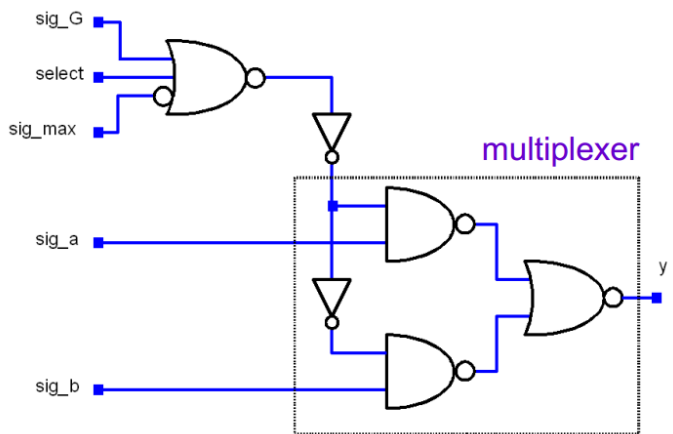

Another synthesis result

 


Quartus synthesis result

Synthesis: Continuous Assignment

A conditional operator assigns the value *z* to the right-hand side expression of a continuous assignment will synthesize to a three-state device.
 
```
module udp (y_out, sel, data);  
output [3:0] y_out;  
input [3:0] data;  
input sel;  
assign y_out = sel ? data : 4'bz;  
endmodule
```



Synthesis: Level-sensitive cyclic behavior

A level-sensitive cyclic behavior will synthesize to combinational logic if it assigns a value to each output for every possible value of its inputs.


- The event control expression of the behavior must be sensitive to every input
- Every path of the activity flow must assign value to every output.

```
module comparator (a_gt_b, a_lt_b, a_eq_b, a, b);
  parameter      size = 2;
  output          a_gt_b, a_lt_b, a_eq_b;
  input [size: 1] a, b;
  reg             a_gt_b, a_lt_b, a_eq_b;
  integer         k;


  always @ ( a or b) begin: compare_loop
    for (k = size; k > 0; k = k-1) begin
      if (a[k] != b[k]) begin
        a_gt_b = a[k];
        a_lt_b = ~a[k];
        a_eq_b = 0;
      end
      disable compare_loop;
    end
    // if
  end
    // for loop
  a_gt_b = 0;
  a_lt_b = 0;
  a_eq_b = 1;
end
  // compare_loop
endmodule
```

Synthesis: Level-sensitive cyclic behavior

Comparator synthesis result:

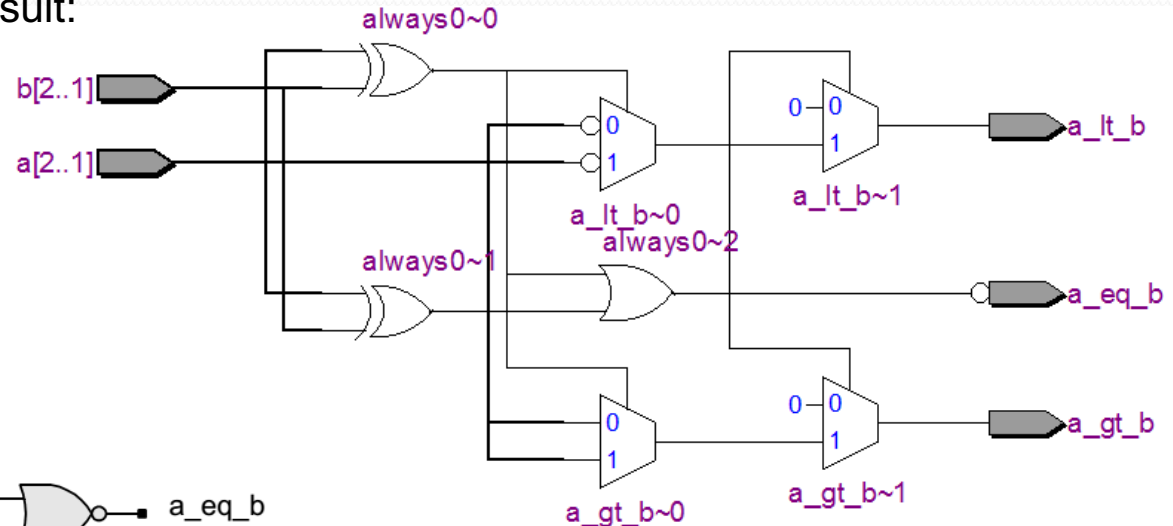

Quartus synthesis result

 


Another synthesis result

Synthesis: Priority structure

- An **if** statement implies higher priority to the first branch than to the remaining branches.
- If branching is mutually exclusive, synthesis produces a mux structure
- Otherwise create a priority structure

```
module mux_4pri (y, a, b, c, d, sel_a, sel_b, sel_c);
  output y;
  input a, b, c, d, sel_a, sel_b, sel_c;
  reg y;

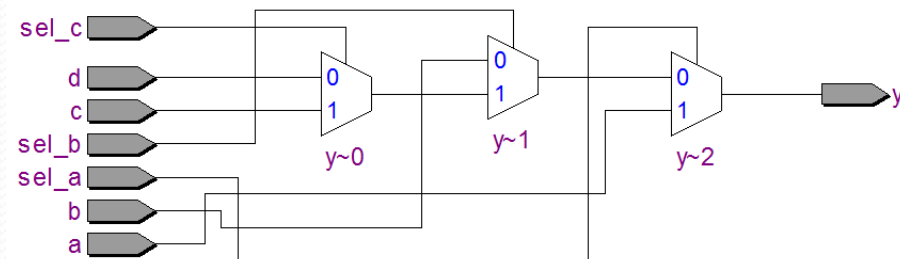  always @ (sel_a or sel_b or sel_c or a or b or c or d)
  begin
    if (sel_a == 1)      y = a; else // highest priority
    if (sel_b == 0)      y = b; else
    if (sel_c == 1)      y = c; else
                        y = d; // lowest priority
  end
endmodule
```



Quartus synthesis result


- Case is synthesized similarly.

Change to $y=1'bx$ (or $1'bz$) -> check synthesis (next slide)


Even when the list of case items is not mutually exclusive a synthesis tool might allow the user to direct that they be treated without priority (e.g., Synopsys *parallel_case* directive).

Exploit don't care condition

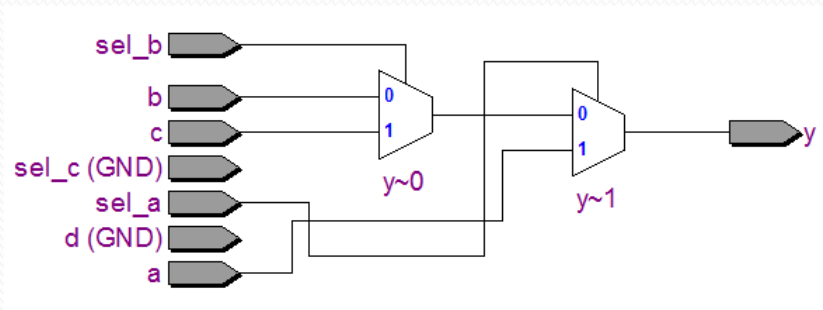An assignment to **x** in a **case** or an **if** statement will be treated as a don't care condition in synthesis.




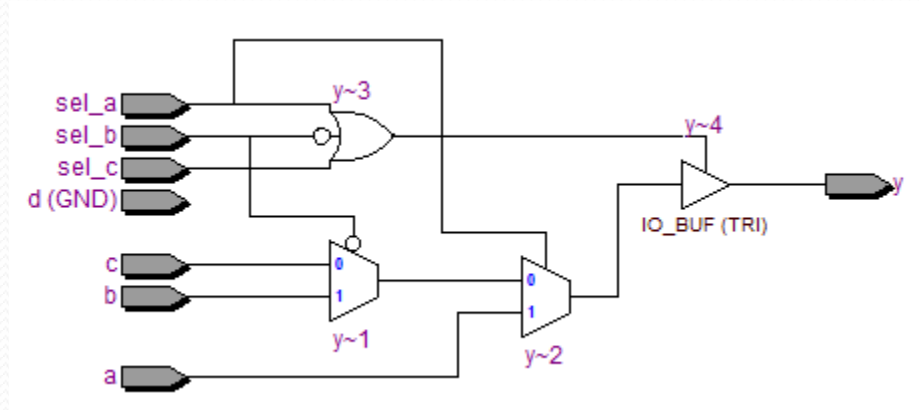An assignment to **z** in **case** or if statement -> tri-state driver




Synthesis ASICs cell

Synthesis Result (With Library Cells)

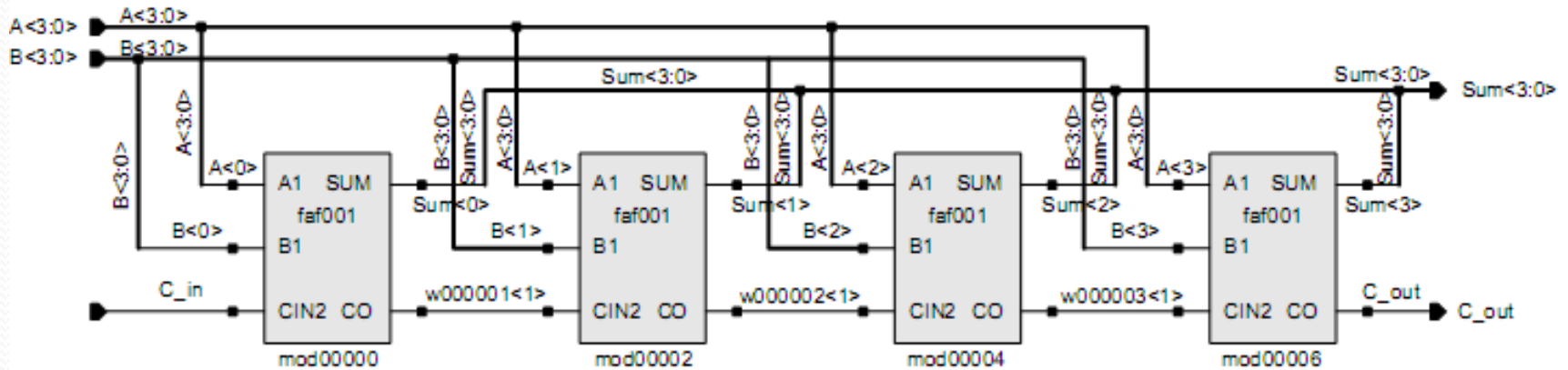

An alternative implementation

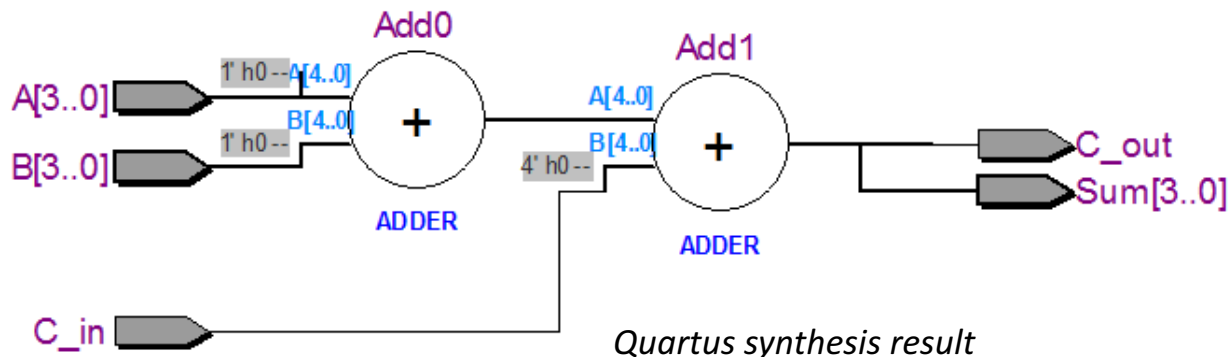

Synthesis: Resource sharing

- If the dataflow within the behavior do not conflict, the resource can be shared between one or more paths


```
assign y_out = sel ? data_a + accum : data_a + data_b;
```

Consequently, the operators can be implemented by a shared adder whose input data-paths are multiplexed. This feature is vendor-dependent. If the tool does not automatically implement resource sharing, the description must be written to force the sharing.


- The use of parentheses in the description in **res_share** forces the synthesis tool to multiplex the datapath

```
module res_share (y_out, sel, data_a, data_b, accum);  
  output [4: 0]    y_out;  
  input   [3: 0]    data_a, data_b, accum;  
  input                sel;  
  
  assign y_out = data_a + (sel ? accum : data_b);  
endmodule
```

Synthesis: Resource sharing

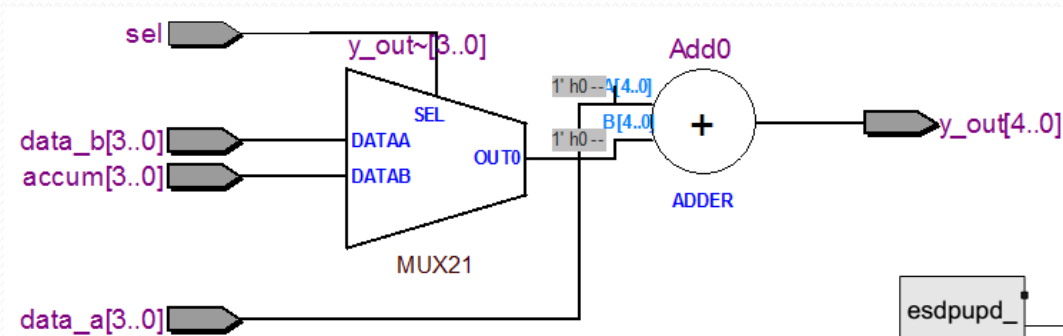

Quartus synthesis result

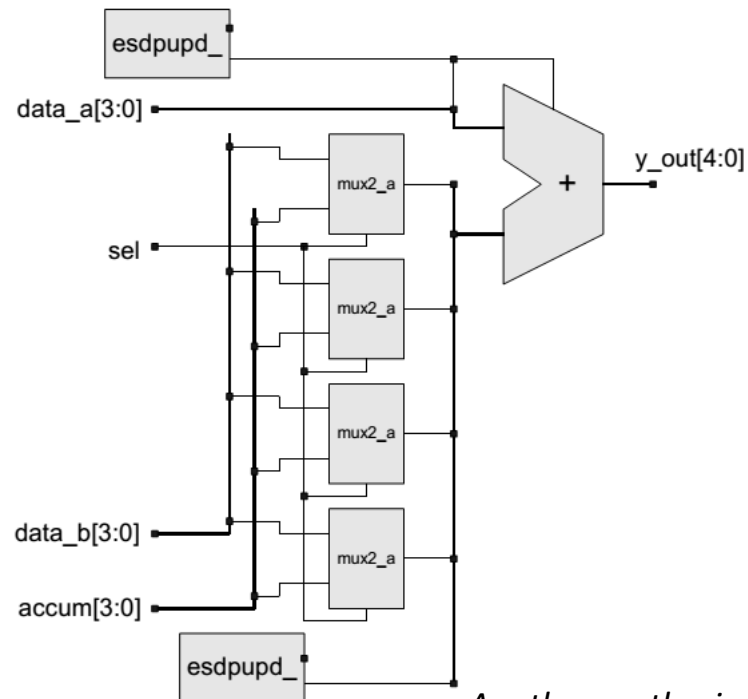

Another synthesis result

Synthesis of sequential logic with latch

- A set of feedback –free netlist of combinational primitives will synthesize into latch-free combinational logic.
- A set of feedback –free netlist of continuous assignments will synthesize into latch-free combinational logic.
- A continuous assignment with feedback in a conditional operator will synthesize into a latch.

```
assign data_out = (CS_b == 0) ? (WE_b == 0) ? data_in : data_out : 1'bz;
```


Synthesis of sequential logic with Latch

- Accidental synthesis of Latch
- Intentional synthesis of Latch

Accidental synthesis of Latch

- A Verilog description of combinational logic must assign value to the outputs for all possible values of the inputs.
- Incomplete specification infers Latch
 
```
module mux_latch (y_out, sel_a, sel_b, data_a, data_b);  
  output      y_out;  
  input       sel_a, sel_b, data_a, data_b;  
  reg         y_out;  
  
  always @ ( sel_a or sel_b or data_a or data_b )  
    case ({sel_a, sel_b})  
      2'b10: y_out = data_a;  
      2'b01: y_out = data_b;  
    endcase  
endmodule
```




A synthesis result

Intentional synthesis of Latch

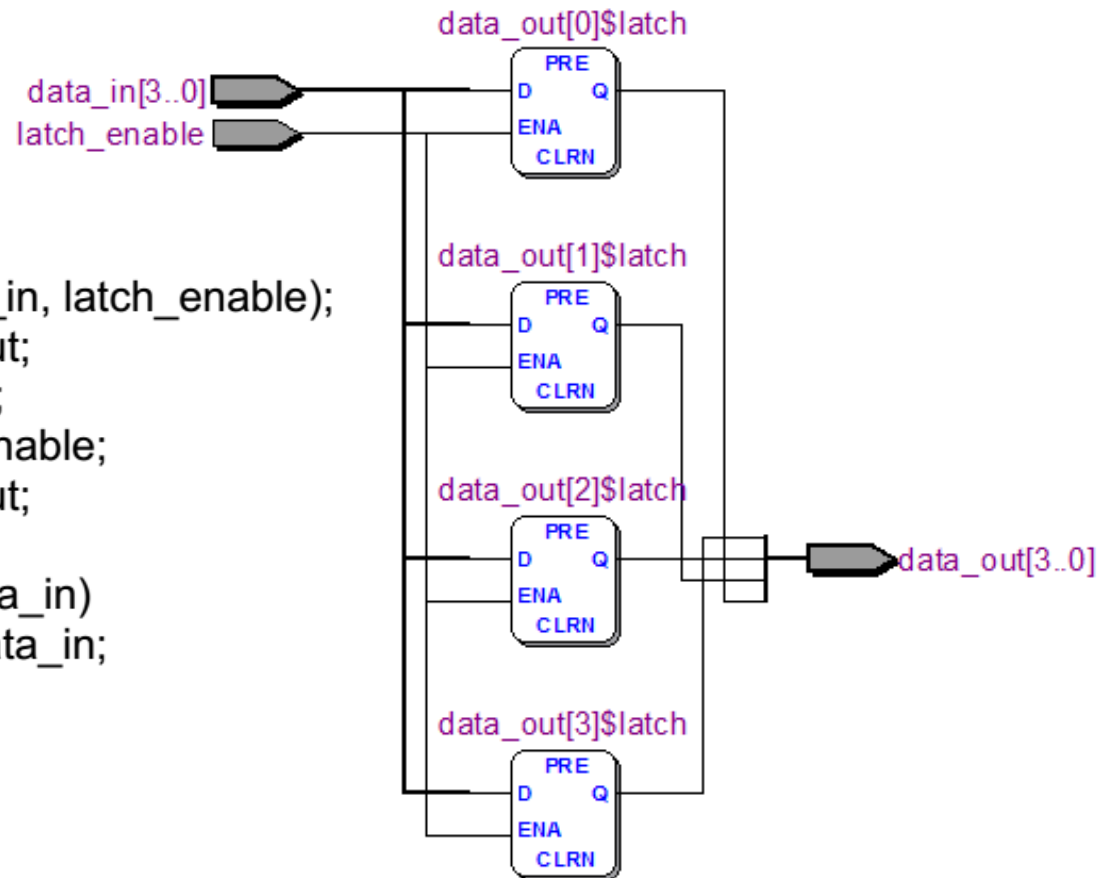Example:

```
module latch_if1(data_out, data_in, latch_enable);  
  output      [3: 0]    data_out;  
  input       [3: 0]    data_in;  
  input       [3: 0]    latch_enable;  
  reg         [3: 0]    data_out;  
  
  always @ (latch_enable or data_in)  
    if (latch_enable) data_out = data_in;  
    else data_out = data_out;  
endmodule
```



Synthesis of sequential logic with flip-flops

❖ Flip-flop or Latch

- Memory inferred for an edge-sensitive cyclic behavior will be synthesized as a flip flop
- Memory inferred for a level-sensitive cyclic behavior or a continuous assignment with feedback will be synthesized as a latch
- Note: an incomplete conditional statement (***if...else***) or a **case** statement in a level-sensitive cyclic behavior will synthesize to a latch.
- Note: an incomplete conditional statement statement (***if...else***) or a **case** statement in an edge-sensitive cyclic behavior will synthesize to a flip-flop with circuitry effectively implementing clock enable.

Synthesis of sequential logic with flip-flops

❖ Synchronizing signal

- The order in which signals appear in the event control expression of an edge-sensitive cyclic behavior does not determine which signal is the synchronizing signal
- The sequence in which signals are decoded in the statement that follows the event control expression of an edge-sensitive cyclic behavior determines which of the edge-sensitive signals are control signals and which is the clock (i.e., the synchronizing signal).

Note: If the event control expression is sensitive to the edge of more than one signal, an ***if*** statement must be the first statement in the behavior.

Synthesis of sequential logic with flip-flops

Example: Synthesis
of a 4-bit Parallel
Load Data Register


```
module D_reg4_a (Data_out, clock, reset, Data_in);
  output [3: 0] Data_out;
  input [3: 0] Data_in;
  input clock, reset;
  reg [3: 0] Data_out;

  always @ (posedge clock or posedge reset)
  begin
    if (reset == 1'b1) Data_out <= 4'b0;
    else Data_out <= Data_in;
  end
endmodule
```

- The positive edge of *reset* appears in the event control expression and appears in the first clause of the *if* statement
- The positive edge of *clock* also appears in the event control expression, but is not explicitly decoded by the branch statement that follows the event control expression.

Synthesis of sequential logic with flip-flops

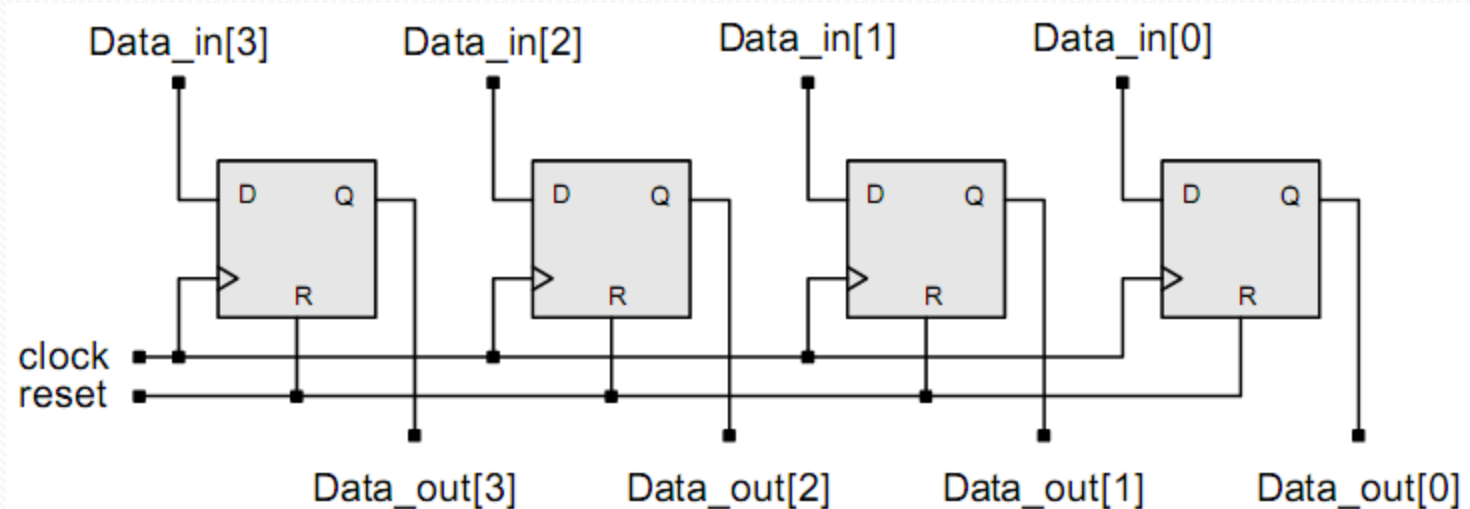Example: Synthesis
of a 4-bit Parallel
Load Data Register




A synthesis result

Synthesis of sequential logic with flip-flops

Another example:
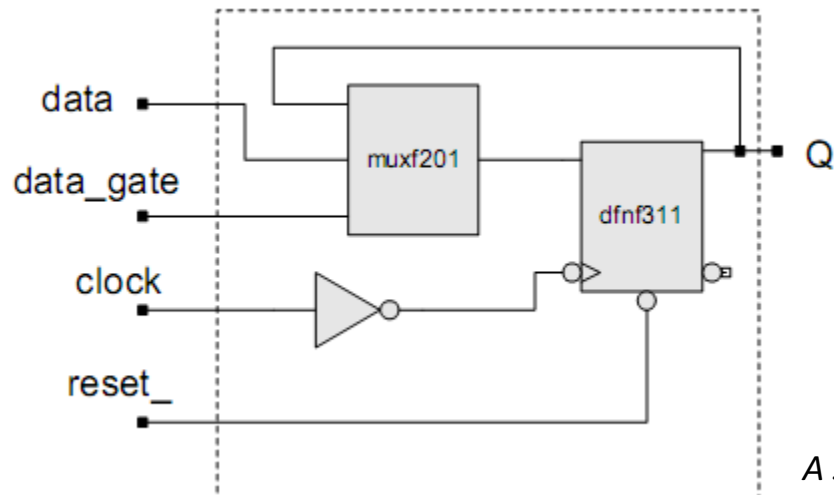
```
module best_gated_clock (clock, reset_, data_gate, data, Q);  
  input      clock, reset_, data, data_gate;  
  output     Q;  
  reg        Q;  
  
  always @ (posedge clock or negedge reset_)  
    if (reset_ == 0) Q <= 0; else if (data_gate) Q <= data;  
endmodule
```



A synthesis result


Synthesis tip

A variable that is referenced within an edge-sensitive behavior before it is assigned value by the behavior will be synthesized as the output of a flip-flop.

```
module swap_synch (data_a, data_b, set1, set2, clk); // Typo at text
  output      data_a, data_b;                      // Typo at text
  input       clk, set1, set2;
  reg         data_a, data_b;

  always @ (posedge clk)
  begin
    if (set1) begin data_a <= 1; data_b <= 0; end else
    if (set2) begin data_a <= 0; data_b <= 1; end else
    else
      begin
        data_b <= data_a;
        data_a <= data_b;
      end
    end
  end
endmodule
```

Synthesis tip

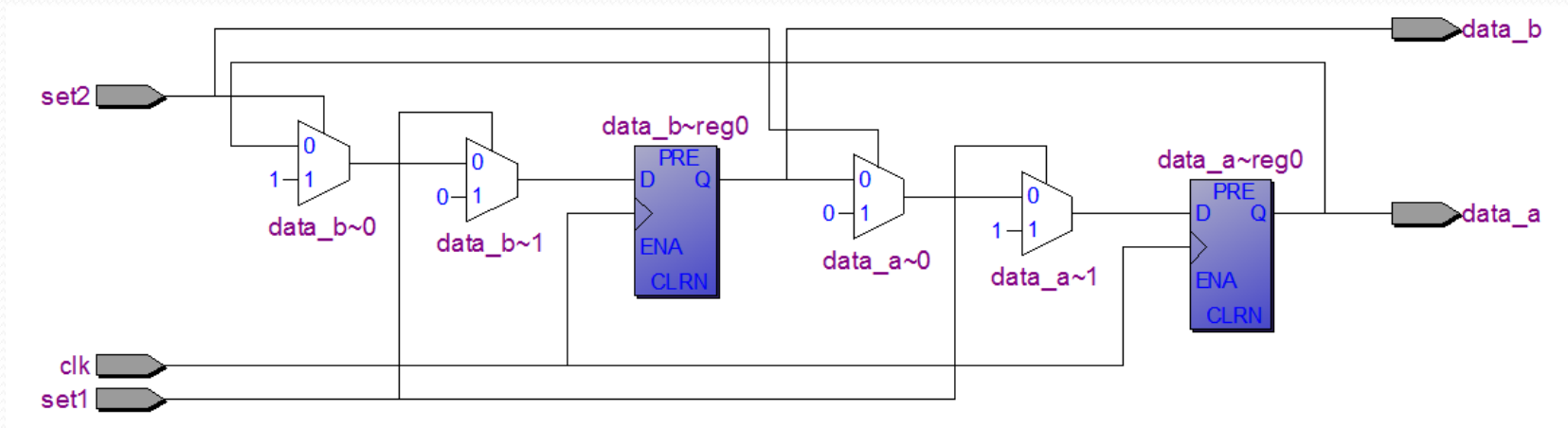

A synthesis result

Synthesis tip

A variable that is assigned value by a cyclic behavior before it is referenced within the behavior, but is not referenced outside the behavior, will be eliminated by the synthesis process.

```
module or4_behav (y, x_in);  
    parameter    word_length = 4;  
    output        y;  
    input         [word_length - 1: 0] x_in;  
    reg           y;  
    integer       k; // Eliminated in synthesis  
  
    always @ x_in  
    begin: check_for_1  
        y = 0;  
        for (k = 0; k <= word_length - 1; k = k+1)  
            if (x_in[k] == 1) begin  
                y = 1;  
                disable check_for_1;  
            end  
        end  
    end  
endmodule
```

Synthesis tip

D_out is not referenced outside the scope of the behavior
A synthesis tool will eliminate *D_out*. output of a flip-flop.

```
module empty_circuit (D_in, clk);  
  input  D_in;  
  input  clk;  
  reg    D_out;  
  
  always @ (posedge clk) begin  
    D_out <= D_in;  
  end  
endmodule
```

Note: If *empty_circuit* is modified to declare *D_out* as an output port, *D_out* will be synthesized as the output of a flip-flop.

Synthesis of Data types

- The identity of nets that are primary inputs or outputs are retained in synthesis
- Internal nets may be eliminated by synthesis
- Integers are stored as 32-bit words (minimum per IEEE 1364)
- Used sized parameters rather than integer parameters

Synthesis of Operators

Some operators may map directly into library cells (e.g. +, 1, <, >, =)
Synthesis might impose restrictions on an operator

- Shift operators is allowed only if the shift index is a constant
- Reduction, bitwise, and logical operators synthesize to equivalent gates
- Conditional operator synthesizes to a mux structure
- If both operands of * are constant the tool produces the constant result
- If one operand of * is a power of 2 the synthesis tool forms the result by left-shifting the other operand
- If one operand of / is a power of 2 the result will be formed by right-shifting the other operand

Synthesis of Operators

Use parentheses within expressions to influence the outcome of synthesis

```
module operator_group (sum1, sum2, a, b, c, d);  
  output [4: 0]    sum1, sum2;  
  input  [3: 0]    a, b, c, d;  
  
  assign sum1 = a + b + c + d;  
  assign sum2 = (a + b) + (c + d);  
  
endmodule
```

Synthesis results:

